

4. *Design With Verilog*

Dr. Paul D. Franzon

Outline

1. Procedural Examples
2. Continuous Assignment
3. Structural Verilog
5. Common Problems
6. More sophisticated examples

Always Design Before Coding

4.1 Procedural Code

Dr. Paul D. Franzon

Outline

1. Literals
2. Flip-flops
3. Behavioral logic descriptions

References

1. Quick Reference Guide
2. Ciletti, Ch. 4-6
3. Smith & Franzon, Chapter 2-6, 8, Appendix A

Objectives

Objectives:

- Describe how to represent numbers in Verilog.
- Understand why non-blocking assignment should be used when flip-flops are being inferred.
- Describe how some of the different types of flip-flops can be represented in Verilog.
- Describe how to capture complex combinational logic in procedural blocks, including encoders and decoders .
- Identify how to represent latches in procedural blocks, both intentionally and unintentionally.
- Understand how don't cares are used in procedural blocks.
- Identify when a for loop is appropriate to use when describing combinational logic.

Motivation

Motivation:

- Enrichen your knowledge of synthesizable Verilog that can be described procedurally
- Justify use of “<=“ when assigning to flip flops
- Capturing the behavior of a complex logic block in a procedural assignement can be very useful


References

- Ciletti:
 - Inside front cover : Summary
 - Sections 5.6, 5.7: Flip-flops
 - Section 5.8: Procedural code examples
 - Sections 6.2: Synthesis of various blocks (priority, don't cares)
 - Appendix C : Verilog Data Types
 - Appendix G.6 G.7 : Explains assignment and simulator operation
 - Appendix H: Flip-flops
 - Appendix I: Verilog 2001
- Smith and Franzon
 - Sections 2.1, 2.2 : Datatypes
 - Chapter 5: Procedural code
- Sutherland Reference guide: Good crisp refresher

Revision

- Draw logic and a timing diagram corresponding the following code extracts:


```
// all variables are 1-bit wide
```

 

```
always@ (A)
```

```
  E = ~A;
```

```
assign D = C ^ E;
```

 

Specifiying Numbers in Verilog

Logic values:

Logic Value	Description
0	Zero, low, or false
1	One, high or true
Z or z or ?	High impedance, tri-stated or floating
X or x	Unknown, uninitialized, or Don't Care

Integers:

`1'b1;` `4'b0;`

size 'base value ; size = # bits, HERE: base = binary

Other bases: h = hexadecimal, d = decimal (which is the default)

Examples: 10 00 .. 01010 3'd5 101
 8'hF0 11110000 8'hF 00001111
 5'd11 01011 2'b10 10

High order bits are truncated if the size is smaller


Unspecified high order bits are zero-filled if left most bit is 0 or 1

Default is 32-bit decimal

Specifying Numbers

Special Values

 - x = don't care or unknown
- z = high impedance (not driven to a specific value)



S	D	out
0	0	floating (z)
0	1	floating (z)
1	0	1
1	1	0

- x and z are self-extending if they are the left most bit
- 8'bx0: xxxx_xxx0
- 3'bz: zzz

Underscore is ignored

Verilog 2001 Syntax

- *Signed Values:*
<size>'s<base format><value>
- The “s” denotes that a value is signed (all other values are assumed unsigned)
- This does not change the value, but it does change how operators (+, <<<, etc.) deal with the value (namely, whether or not it will be sign-extended after the operation)
- Examples:
 - 4'hF = 1111 in binary
 - 4'shF = 1111 in binary (but will sometimes be interpreted as -1)
 - 6'shF = 001111 (does not change extension rules)

More on Numbers

- Though Verilog is liberal in terms of autotruncating numbers, some synthesis tools are not
 - E.g. `A = B ? 1 : 0;`
 - ◆ will simulate fine but synopsys will interpret 1 as a signed number
 - Better solution: `A = B ? 1'b1 : 1'b0;`
 - Also outputs that are assigned with excess bits may result in synthesis warnings
 - ◆ E.g.
 `output reg [4:0] A;`
 `...`
 `A = {B; 3};`
 might also produce synthesis warnings
 `A = {B, 2'h3};`
 would be better

Other Lexical Conventions

- Spaces, underscores and new lines are ignored
 - Eg. Write 8 bits as 0101 1111 to make more readable
- Verilog is CaSe sEnsitive
- Identifiers have to start with a character (A-Z, a-z) and may only contain characters, numbers, _ and \$
- Verilog reserved words can not be used for variables,
 - E.g. always, module, etc.

Vectors

In RTL most variables are vectors of bits

Vectors can be specified by declaring the range of bit numbers with the variable name. The form of the declaration is:

[<high>: <low>] <variable> ;
or [<low>: <high>] <variable> ;

```
wire [7:0] BYTE; // declare 8-bit data named BYTE
reg [15:0] INFO; // declare 16-bit register named INFO
reg [0:11] DATA; // declare 12-bit register named DATA
```

- Left bit is considered the most significant
- By convention, use [<high>:<low>] (Little Endian)*
 - DATA[0] is the left most, most significant bit

*According to VL standard, this format is actually Little not Big Endian. I edited slide but not the recording. It does not matter as long as you use one consistently.

Specifying Parts of Vectors

Given vector declarations, it is possible to reference parts of a register (down to a single bit). The format of the reference follows the pattern `<vector> [<bit range>]`.

INFO [5]	// bit 5 of INFO
INFO [11:8]	// bits 11-8 of INFO (bits 11-8)
DATA [7:0]	// least significant byte of DATA

Other Types

- Arrays (1-D and 2-D arrays of vectors)
 - Example: `reg [15:0] RegisterFile [0:31]; // 32 x 16-bit vectors`
 - Note arrays can NOT be passed through input/output ports
 - In synthesizable design:
 - ◆ 1-D arrays used to model register files and un-synthesized memories
 - ◆ 2-D arrays have little relevance
 - Integer `//` used as a loop counter
- Not used in synthesis but useful in test fixture:
- Real
 - Time (accessed w/ system function `$time`)
 - See Sutherland, section 7.0 for details

Summary

- Lexical rules are specified so that numbers can be precisely enumerate size'base value
- All signals in synthesizable Verilog are bits or vectors of bits
- Do exercise before proceeding to next sub-module

Procedural Blocks

Code of the type

```
always@(input1 or input2 or ...)  
begin  
    if-then-else or case statement, etc.  
end
```

is referred to as *Procedural Code*

- Statements between **begin** and **end** are executed *procedurally*, or in order.
- Variables assigned (i.e. on the left hand side) in procedural code must be of a register data type. Here type `reg` is used.
 - Variable is of type `reg` does NOT mean it is a register or flip-flop.
- The procedural block is executed when triggered by the `always@` statement.
 - The statements in parentheses (. . .) are referred to as the *sensitivity list*.

Blocking and Non-blocking Assignment

- Or WHY I always use “<=” for flip-flops
- Blocking (“=”)

```
always@ ( )
begin
    A = B;
    B = A;
end
```

**Execution of next statement
“blocked” until this statement is
completed. i.e Statements execute
sequentially.**

- Non-Blocking (“<=”)

```
always@ ( )
begin
    A <= B;
    B <= A;
end
```

**Execution of next statement NOT
“blocked”. i.e Statements execute as
if they were being run in parallel.**

Assignment

- Assuming A=3; B=4; before execution, determine their values after execution

- Blocking (“=”)

```
always@(posedge clock)
begin
    A = B;
    B = A;
end
```

A = 4;
B = 4;
i.e. B took the value A
would have AFTER the
posedge clock

- Non-Blocking (“<=“)


```
always@(posedge clock)
begin
    A <= B;
    B <= A;
end
```

A = 4;
B = 3;

Assignment

- Now draw the logic each describes
- Blocking (“=”)
 
```
always@(posedge clock)
begin
    A = B;
    B = A;
end
```




B has same value as A after clock event is over → B connected to input of A

- Non-Blocking (“<=“)

```
always@(posedge clock)
begin
    A <= B;
    B <= A;
end
```

Always use “<=“ with flip-flops

 

Examples

- Describe logic and draw timing for the following:

// all variables are 1-bit wide

```
reg B, D, E;
```

```
always@(posedge clock)
```



```
    B <= A ^ C;
```

```
always@(posedge clock)
```

```
    D <= A | C;
```

```
always@(posedge clock)
```

```
    E <= B & D;
```

  

... Examples

- Will the following produce the same logic?

```
// all variables are 1-bit wide
```

```
reg B, D, E;
```

```
always@(posedge clock)
```

```
begin
```

```
    B <= A ^ C;
```

```
    D <= A | C;
```

```
    E <= B & D;
```

```
end
```

Yes

... Examples

- Will the following produce the same logic?

// all variables are 1-bit wide

```
reg B, D, E;
```

```
always@(posedge clock)
```

```
begin
```


```
    B = A ^ C;
```

```
    D = A | C;
```

```
    E = B & D;
```

```
end
```

No

 

Blocking vs. Non-Blocking

- Which describes better what you expect to see?
 - Non-blocking assignment
- Note:
 - Use non-blocking for flip-flops
 - Use blocking for combinational logic
 - ◆ Logic can be evaluated in sequence – not synchronized to clock
 - Don't mix them in the same procedural block

Combinational Logic

- Procedural description of combinational logic can be very useful
 - Can describe **structure** or **behavior** of logic block
 - ◆ If you are just describing structure, consider continuous assignment instead
 - Always uses blocking assignment
 - ◆ Example. Consider (B, C, E are outputs of flip-flops)

```
always@ (*)
```

```
begin
```

```
    A <= B & C;
```

```
    D <= A & E;
```

```
end
```

D needs the value of A that existed BEFORE this block was triggered. i.e. This might be the value of A from the previous clock cycle. This is not simple to work out how to obtain.

```
always@ (*)
```

```
begin
```

```
    A = B & C;
```

```
    D = A & E;
```

```
end
```

A changes then D changes. I.e. A is an input of the second AND

Registers

Some Flip Flop Types:

```
reg    Q0, Q1, Q2, Q3, Q4;

// D Flip Flop
always@(posedge clock)
    Q0 <= D;

// D Flip Flop with asynchronous reset
always@(posedge clock or negedge reset)
    if (!reset) Q1 <= 0;
    else Q1 <= D;

// D Flip Flop with synchronous reset
always@(posedge clock)
    if (!reset) Q2 <= 0;
    else Q2 <= D;

// D Flip Flop with enable
always@(posedge clock)
    if (enable) Q3 <= D;

// D Flip Flop with synchronous clear and preset
always@(posedge clock)
    if (!clear) Q4 <= 0;
    else if (!preset) Q4 <= 1;
    else Q4 <= D;
```

Note:

Registers with asynchronous reset are smaller than those with synchronous reset

+ don't need clock to reset

+ easier to integrate with test features.

Reset is a global signal intended to get the chip into a known state. It is not to be locally generated or modified.

Reset

- Reset is an important part of the control strategy
 - Used to initialize the chip to a known state
 - Distributed to registers that determine state
 - E.g. FSM state vector
 - Usually asserted on startup and reset
 - Globally distributed
 - Not a designer-controlled signal



Summary


- Always use non-blocking assignment (" \leq ") when assigning to flip-flops
 - Even if you don't think it is needed – Makes code easier to maintain
- Always use blocking assignment (" $=$ ") when describing combinational logic
- Apply a global reset signal to all registers that determine machine "state"
 - FSMs, some counters, some status registers, etc.
- Reset is a global signal coming from outside the digital design
 - Not to be modified or locally generated

- Proceed to sub-module quiz and next sub-module

Behavior → Function


What do the following code fragments synthesize to?

```
reg foo;  
always @(a or b or c)  
begin  
    if (a)  
        foo = b | c;  
    else foo = b ^ c;  
end
```

 

```
reg foo;  
always@(clock or a)  
    if (clock)  
        foo = a;  
end
```


Latch

 

Avoid unintentional latches

Example:

```
reg foo;  
always @(a or b or c)  
begin  
    if (a)  
        foo = b | c;
```

 

a could be the output of glitchy logic → a glitchy clock, creating unpredictable errors in the actual logic, even if the RTL worked fine pre-synthesis

In a non-clocked procedural block, each variable has to be assigned every time the code is executed, so as not to specify memory, or an unintended latch.

Case statement

- What about this statement?

```
reg [1:0] B;  
always@(*)  
  case (A)  
    2'b00 : B = C;  
    2'b01 : B = D;  
    2'b10 : B = E;  
    default : B = F;  
  endcase
```

Evaluate () against statements on LHS of :

Potential matches evaluated in SEQUENCE.

Statement on RHS executed upon match.

Default statement executed if no other match occurs (default optional)


After statement on RHS executed, jump to end.

Here default is needed to prevent latches

Case statement

- What logic behavior does it simulate? I.e. What would it build?

 
```
reg [1:0] B;  
always@(*)  
  case (A)  
    2'b00 : B = C;  
    2'b01 : B = D;  
    2'b10 : B = E;  
    default : B = F;  
  endcase
```



Case statement

- Casex permits matches against z (high impedance) and x (don't care)
- E.g.
 
```
reg [1:0] B;  
always@(*)  
  casex (A)  
    2'b00 : B = C;  
    2'b01 : B = D;  
    2'b1x : B = E;  
  endcase
```




Note: No “unknown” (x) in actual design

Priority Encoder

- What does the following specify?

```
always@(A or B or C)
  casex(A)
    3'b1xx : out = B;
    3'bx1x : out = C;
    default : out = 2'b0;
  endcase
```

 **A[2] has priority over other bits of A.
If A[2]=1, out=B, no matter what.**




- Rewrite as if-else

```
always@(A or B or C)
  if (A[2]) out = B;
  else if (A == 3'b01x) out = C;
  else out = 2'b0;
```

Demultiplexer

 - Demultiplexer (demux) activates one or more outputs depending on an input and control signal.
 - Often used for Decoders
- Write Verilog for:



```


always@ (*)
  case (s)
    1'b0: begin
      z0 = in; z1 = 1'b0;
    end
    1'b1: begin
      z0 = 1'b0; z1 = in;
    end
  endcase

```

Decoder

- What does the following specify?
 
```
always@(address)
  case (address)
    2'b00 : line = 4'b0001;
    2'b01 : line = 4'b0010;
    2'b10 : line = 4'b0100;
    2'b11 : line = 4'b1000;
  endcase
```



“one-hot” decoder – only one output line is active at a time

Truth Tables

- If you get stuck how to specify a piece of logic, then simply write its truth table
- THEN capture truth table as a case statement
- Example: **Grey code counter**

- Truth Table:

<i>Count</i>	<i>NextCount</i>
00	: 01
01	: 11
11	: 10
10	: 00
- Code:


```


always@(*)
    casex (Count)
        2'b00 : NextCount = 2'b01;
        2'b01 : NextCount = 2'b11;
        2'b11 : NextCount = 2'b10;
        2'b10 : NextCount = 2'b00;
        2'bxx : NextCount = 2'bxx;
    endcase
      
```

```

always@(posedge clock)
    Count <= NextCount;
      
```

 Exercise

- Write Verilog to capture the following logic:



```
reg [1:0] B,C,D,F;  
reg [3:0] A,E;  
  
always@ (*)  
  case (A[1:0])  
    2'b00: F=B|C;  
    2'b01: F=D;  
    2'b10: F=~E[1:0];  
    2'b11: F=E[3:2];  
  endcase
```

Exercises: Don't Cares in Synthesis

- Real logic can only take on values of 0 or 1
- Don't cares used by Karnaugh map optimizer during synthesis to minimize the logic

```
input [3:0] A;
  reg [1:0] Y;
  always@(A)
    casex (A)
      4'b0001 : Y = 0;
      4'b0010 : Y = 1;
      4'b0100 : Y = 2;
      4'b1000 : Y = 3;
      default : Y = 2'bx;
    endcase
```

		A[1:0]			
		00	01	11	10
A[3:2]	Y[0]				
	00	x	0	x	1
	01	0	x	x	x
	11	x	x	x	x
	10	1	x	x	x



$Y[0] = A[1] \&\& !A[3] \mid \mid A[3]$
 $\&\&$ and $!$ negate $\mid \mid$ or

For loops

```
integer      i, N;
parameter   N=7;
reg         [N:0] A;
always@ (A)
begin
    OddParity = 1'b0;
    for (i=0; i<=N; i=i+1)
        if (A[i]) OddParity = ~OddParity;
end
```

The only valid use of a for loop is to iterate through a fixed array.
If in doubt, don't use.

Unroll the for loop to interpret

  

Note : Parameter to permit bit-width specification.

Notes

- Only `if-then-else`, `case`, `casex`, and `for` loops are useful when specifying the behavior of combinational logic
 - Generally I used `casex` all the time, rather than having to decide between `case` and `casex` – `casex` is more general and quite useful
- Other procedural constructs – `while`, `repeat`, `casez`, `disable` – are not used in synthesizable logic
- `for` has very limited utility
 - If you are using to describe a sequence of steps or an action loop, you are probably using it incorrectly

Exercises

Sketch the truth table, and describe the logic:

```
input [3:0] A;  
reg [1:0] Y;  
always@ (A)  
  casex (A)  
    4'b0001 : Y = 0;  
    4'b0010 : Y = 1;  
    4'b0100 : Y = 2;  
    4'b1000 : Y = 3;  
    default : Y = 2'bx;  
  endcase
```

A	Y
0001	00
0010	01
0100	10
1000	11
All others	xx


4-2 encoder

Note: All the statements here are mutually exclusive – truly parallel statements – no priority implied

 Exercises

Sketch the logic being described:

```
input [1:0] sel;  
input [3:0] A;  
reg Y;  
always@(sel or A)  
  casex (sel)  
    0 : Y = A[0];  
    1 : Y = A[1];  
    2 : Y = A[2];  
    3 : Y = A[3];  
    default : Y = 1'bx;  
  endcase
```



```
wire Y;  
assign Y = A[sel];  
// builds same logic
```

The 'default' here is not essential but useful to
(1) Enforce discipline preventing latches
(2) Ensures proper startup behavior (see later)
Synopsys optimizes it out in this case.

Behavior → Function

Sketch the truth table, and describe the logic:

```
input [3:0] A;
reg [1:0] Y;
always@ (A)
  casex (A)
    4'b1xxx : Y = 0;
    4'bx1xx : Y = 1;
    4'b001x : Y = 2;
    4'b0000 : Y = 3;
    4'b0001 : Y = 0;
    default : Y = 2'bx;
  endcase
```

A	Y
1xxx	00
01xx	01
001x	10
0000	11
0001	00

Priority Encoder
(A[3] has priority over
other bits, etc.)


Behavior → Function

Sketch the logic:

```

input [2:0] A;
reg [7:0] Y;
always@(A or B or C)
begin
  Y = B + C;
  casex (A)
    3'b1xx : Y = B - C;
    3'bx01 : Y = B | C;
    3'b000 : Y = B & C;
  endcase
end

```

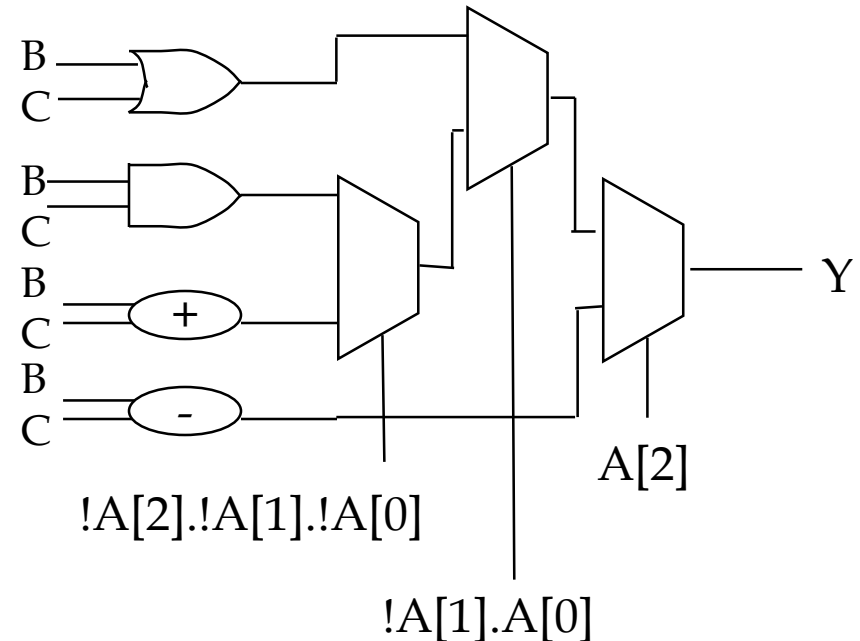*Arithmetic Unit with Priority Decoder*

Starting with $Y=B+C$; prevents unintentional latches much like default does.

Priority Logic

- If the alternatives in the case or if-then-else statement are mutually exclusive, non-priority logic is implied
 - What is synthesized?

A single mux

- Which is faster, priority logic or non-priority logic?

Non-priority (usually)

Exercises

Implement a 2-bit Grey scale encoder: (I.e.
Binary encoding of 1..4 differ
by only 1 bit)

0	00
1	01
2	11
3	10

```
reg [1:0] G;
always@(in)
case (in)
    2'h0 : G = 2'b00;
    2'h1 : G = 2'b01;
    2'h2 : G = 2'b11;
    2'h3 : G = 2'b10;
    default : G = 2'bxx;
endcase
```

Implement hardware that counts the # of 1's in
input [7:0] A. Use a for loop

```
reg [3:0] count;
integer i;
always@(A)
begin
    count = 0;
    for (i=0; i<=7; i=i+1)
        count = count + A[i];
end
```

Could also
build truth table
and use a case
statement.

Summary - Behavioral Combinational Logic

- Common constructs

```
always@(*) if else // simple muxes
```

```
always@(*)
```

```
    casex ( )
```

```
        :    ;
```

```
        default : ;
```

```
    endcase
```

```
    // logic that considers multiple alternatives
```

- Less common construct

```
always@(*) for (i..) // iterating through an array
```

- Important to prevent unintentional latches by making sure every variable is assigned no matter how the code is executed

- Goto sub-module quiz and then proceed to first submodule of 4.2